

$$V_{GS2} = V_{DD} - V_O$$

14

$$I_D = k_2 (V_{DD} - V_O - V_{T2})^2$$

uguagliando: $V_O = \left(V_{DD} - V_{T1} + \sqrt{\frac{k_1}{k_2}} V_{T1} \right) - \sqrt{\frac{k_1}{k_2}} V_i$

$$A_v = \sqrt{\frac{k_1}{k_2}} = \frac{dV_O}{dV_i}$$

→ stesso risultato come:

$$I_D = \mu_{n2} V_{GS2}$$


↓

resistenza equivalente di source

$$V_O = \mu_{n1} V_{GS1} \left[\frac{1}{\mu_{n2}} \parallel r_{O1} \parallel r_{O2} \right]$$

$$A_v = \frac{V_O}{V_i} = \frac{\mu_{n1}}{\mu_{n2}}$$

Esempio.

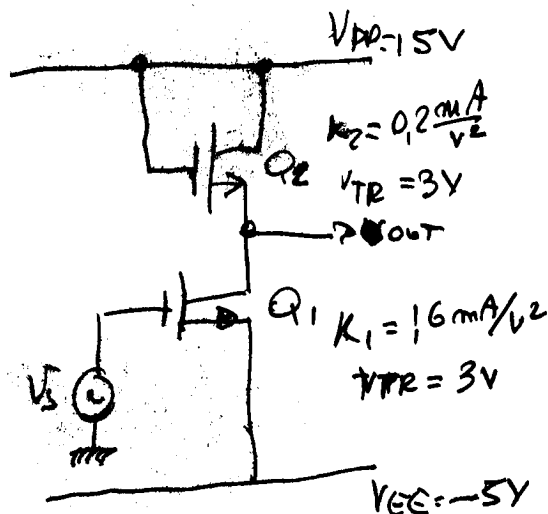

$$V_{GS1} = 5V$$

$$I_{D1} = k_1 (V_{GS1} - V_{TR})^2 = 1.6 (5 - 3)^2 = 6.4 \text{ mA}$$

$$V_{GS2} = \left(\frac{I_{D2}}{k_2} \right)^{1/2} + V_{TR}$$

$$= \left[\left(\frac{6.4}{0.2} \right) \right]^{1/2} + 3V = 8.66 \text{ V}$$

$$V_{OUT} = V_{DD} - V_{GS2} = 15V - 8.66 = 6.34V$$

$$V_{DS1} = V_{OUT} - V_{EE} = 6.34 - (-5V) = 11.34V$$

$$V_{GS1} - V_{TR} = 2V$$