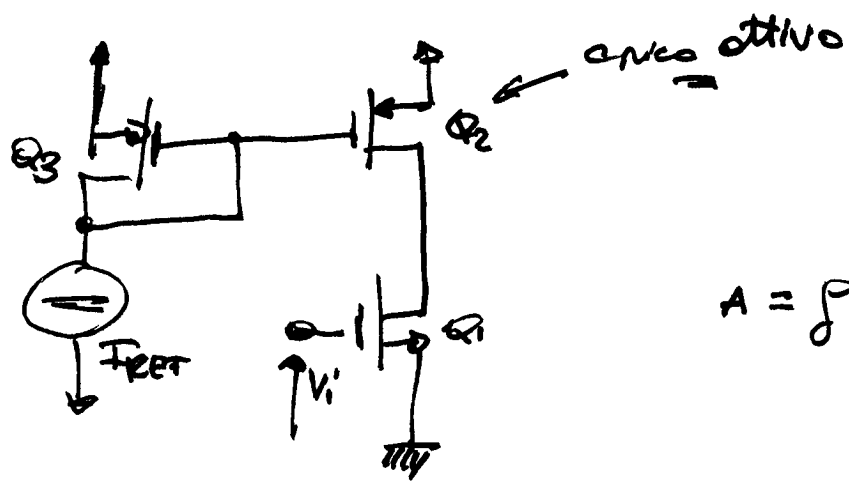


Amplifier circuit



$$A = \beta_{m \beta} [R_{o1} || R_{oe}]$$