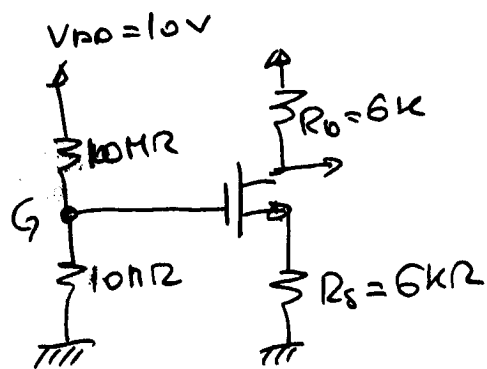




$$V_{th} = 1V \quad K = 0.5 \frac{mA}{V^2}$$


$$V_G = 5V$$

$$\text{se } I_D = 0.5mA \Rightarrow V_S = +3V$$

$$\Rightarrow V_{GS} = 2V \Rightarrow V_D = 7V$$

$$V_{DS} = 4V > (V_{GS} - V_{th})$$

zona di saturazione

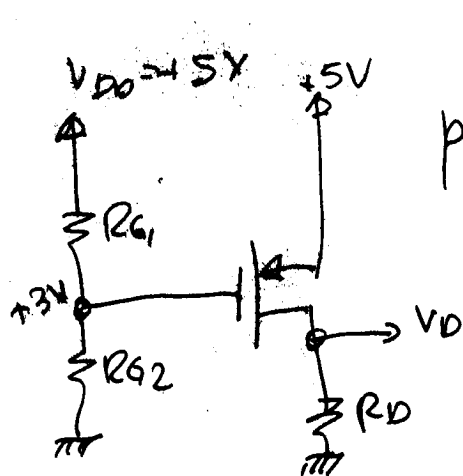


p-MOS

$$I_D = 0.5mA$$

$$V_D = 3V$$

$$V_{th} = -1V$$

$$K = 0.5 mA/V^2$$

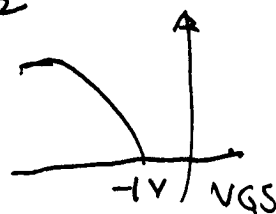

$$0.5 = 0.5 [V_{GS} - (-1)]^2$$

$\Rightarrow V_{GS}$ deve essere negativo nei p-MOS

$$V_{GS} = -2V \Rightarrow V_G = V_{DD} \cdot \frac{R_{G2}}{R_{G1} + R_{G2}}$$

$$\Rightarrow R_{G1} = 2k\Omega \quad R_{G2} = 3k\Omega$$

$$\Rightarrow R_D = \frac{3V}{0.5mA} = 6k\Omega$$