

Esercizio precedente:

8



$$\omega_H = \omega_1 \parallel \omega_2 \quad \frac{1}{\frac{1}{10^4} + \frac{1}{2 \times 10^4}} \sim 0,67 \times 10^4 \frac{\text{rad}}{\text{s}}$$

$$\omega_L = 10 \frac{\text{rad}}{\text{sec}}$$

⇒ potente tecnica per trovare ω_L e ω_H .

medio-banda ⇒ circuito $f(\omega)$ trascurabili

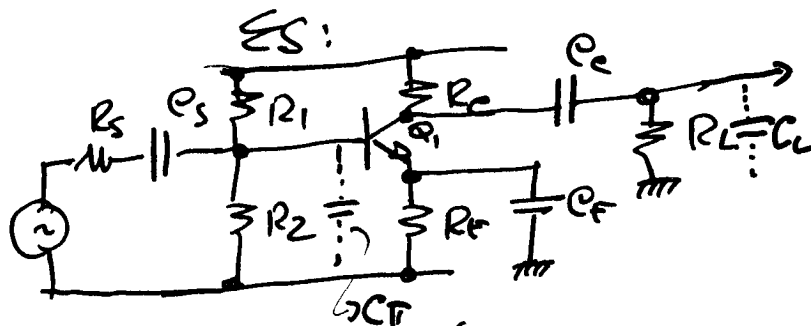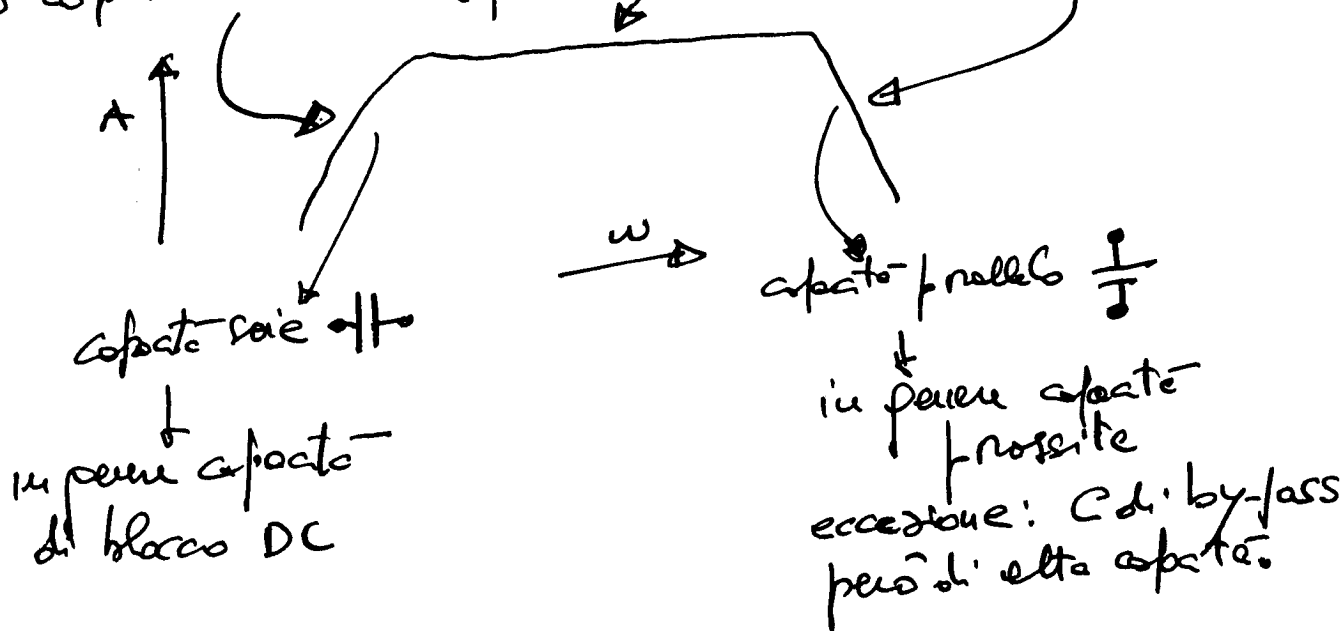⇒ circuito a bassa frequenza } e circuito ad alta frequenza



f_1 e f_2 a bassa frequenza

$$f_1 = \frac{1}{2\pi C_S (h_{fe} R_E \parallel (R_1 \parallel R_2) \parallel R_S)}$$

$$f_2 = \frac{1}{2\pi C_C (R_C \parallel R_L)}$$

C_L (unico)
 C_{CB} ⇒ piccola
 C_{BE}

alte frequenze:

$$f_3 = \frac{1}{2\pi (R_C \parallel R_L) C_L}$$

$$f_4 = \frac{1}{2\pi (h_{fe} R_E \parallel (R_1 \parallel R_2) \parallel R_S) C_{CB}}$$