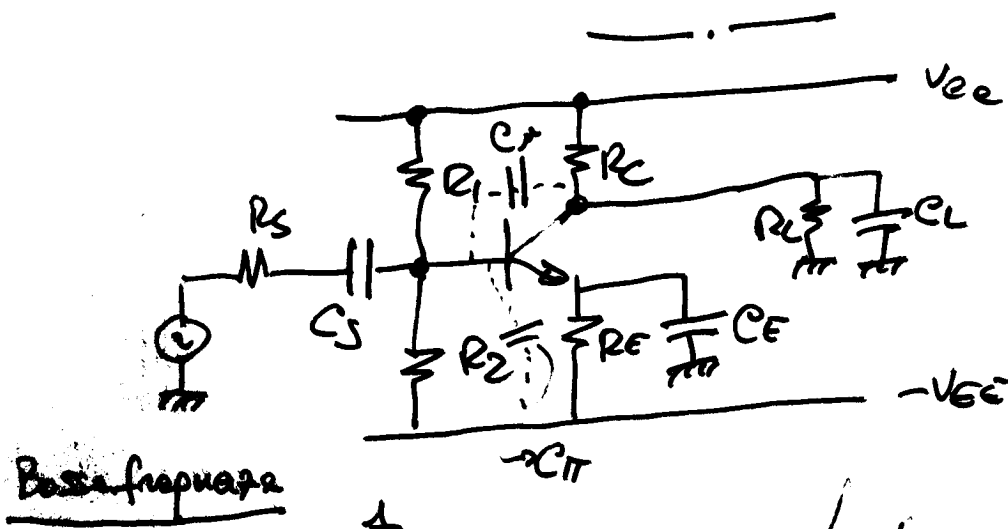


Alta frequenza $\Rightarrow$ C_1 e C_2 in p.p. alternativamente
quasi

$$t_{\pi} = \frac{1}{2\pi(R_S \parallel (R_1 \parallel R_2)) \cdot C_{gs}}$$

$$t_B = \frac{1}{2\pi(R_D \parallel r_o \parallel R_L) \cdot C_L}$$

La più bassa tra t_{π} ed t_B è polo dominante.



Bassa frequenza

$$t_S = \frac{1}{2\pi[R_S + (R_1 \parallel R_2) \parallel h_{fe} \cdot r_e]} \cdot C_S$$


$$t_E = \frac{1}{2\pi[R_E \parallel (r_e \parallel \frac{R_1 \parallel R_2}{h_{fe}})]}$$

$$t_L = t_S + t_E$$

Alta frequenza

$$t_{\pi} = \frac{1}{2\pi(R_S \parallel (R_1 \parallel R_2) \parallel h_{fe} \cdot r_e) \cdot C_{\pi}}$$
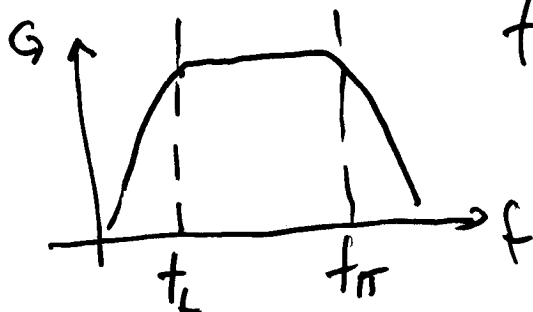
$$t_H = \frac{1}{2\pi(R_E \parallel R_L \parallel R_D) \cdot C_L}$$



$$t_H = t_{\pi} \parallel t_M = \frac{t_{\pi} \cdot t_M}{t_{\pi} + t_M}$$

* Aggiungere in $t_{\pi} \cdot C_{\pi} + A C_L$

$\hookrightarrow$ Effetto Miller
Cin distribuite da base