

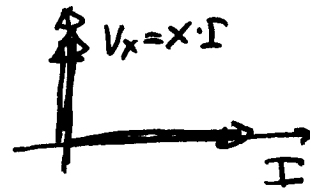


ωL indicate con X_L prende il nome di reattanza ⁸
induttiva. Invece di prendere vettoriali i usano
valori efficaci $I = \frac{I_H}{\sqrt{2}}$ $V = \frac{V_H}{\sqrt{2}}$

$$\vec{V}_x = jX \vec{I}$$

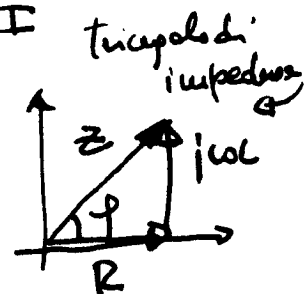

Circuito ohmico-induttivo

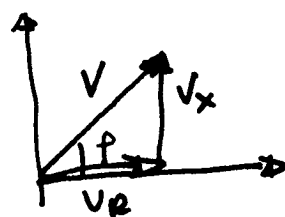


$$\vec{V}_R = R \cdot \vec{I}$$

$$\vec{V}_x = jX \vec{I}$$

$$X = \omega L \quad Z = R + j\omega L$$

$$\text{impedenza } Z = \sqrt{R^2 + X^2}$$

$$\tan \phi = \frac{X}{R}$$

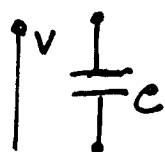


$$q = C \cdot V$$

$$i = \frac{dq}{dt}$$

$$i = C \frac{dV}{dt}$$


in alternata: $\vec{V} = V e^{j\omega t}$
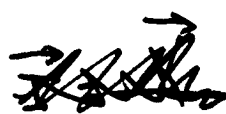
$$\vec{I} = \frac{d}{dt} \vec{q}(t) \cdot C = \left[\frac{d}{dt} [V e^{j\omega t}] \right] = j\omega C V e^{j\omega t} = j\omega C \vec{V}$$



$$\frac{\vec{I}}{j\omega C} = \vec{V}$$

$$X_C = \frac{1}{j\omega C}$$

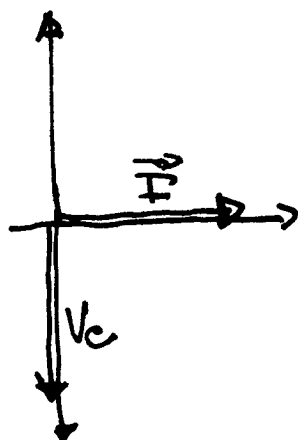

X_C = reattanza capacitiva = reazione di induttanza
alternanza di carica e scarica in C

convertita in C in anticipo di 90° su V_C
in termini di valori efficaci

$$I = \frac{V_C}{\frac{1}{\omega C}}$$

Potenza reale = 0