
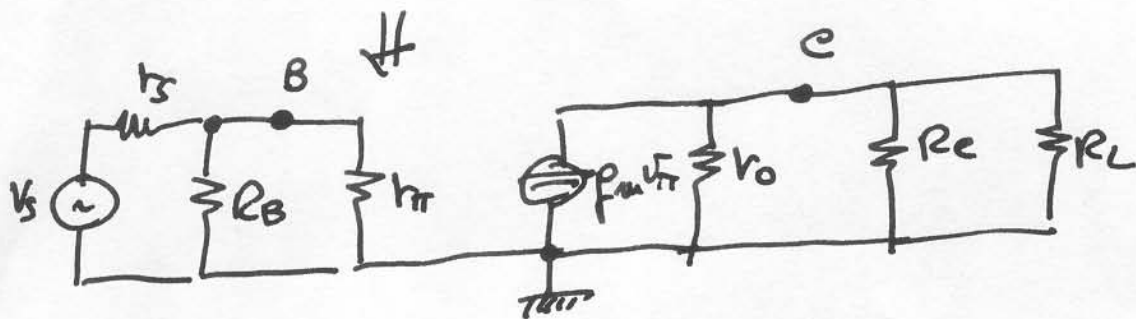


Configurazioni.

8/5/1

ba emittente comune.

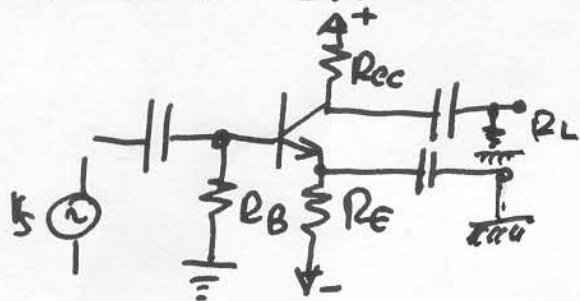

$$R_i = R_B \parallel r_{\pi}$$

$$R_o = R_C \parallel r_o$$

$$r_{\pi} = r_e \cdot \beta$$

$Z_{in} \Rightarrow$ moderate input impedance ($R_B \parallel r_{\pi}$)

transconductance g_m

$$Z_{out} \Rightarrow R_C \parallel r_o$$